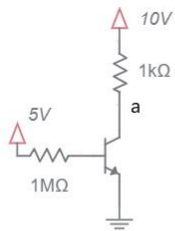





## DC circuits with NPN BJTs and resistors

Determine the voltage at the labeled nodes. Determine collector, base and emitter currents.


- If the BJT is in the active region, assume  $V_{be} = 0.7V$ ,  $\beta = 100$ , and  $i_c = i_e$ .
- If the BJT is in saturation, assume that  $V_{ce} = 0.2V$ .
- Only compute  $\beta$  when the BJT is in saturation.
- Write your answers on the table shown on the page following the problems.
- On separate page(s), show your work for each problem. Denote the operating region of BJTs by writing ACT/SAT next to active/saturated mode BJTs respectively.
- Write "unknown" for circuits whose current/voltage cannot be determined.
- Round your answer to 2-significant figures and include units.




001

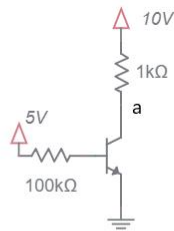


002

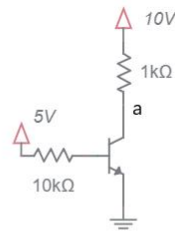


003

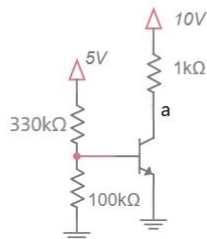


004

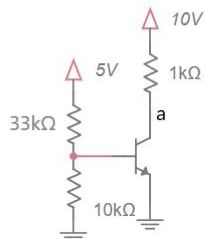


005

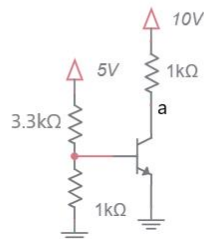


006

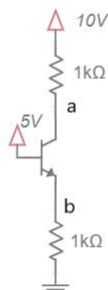









007

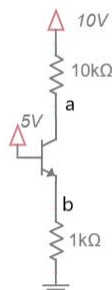

008

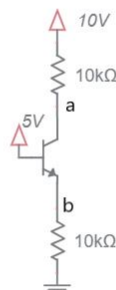

009

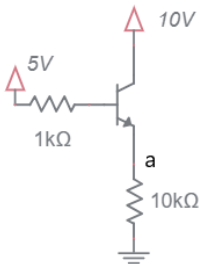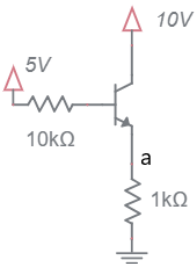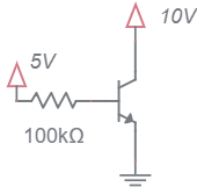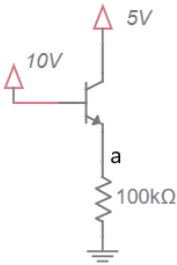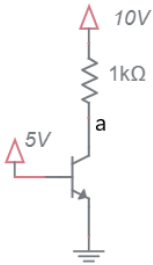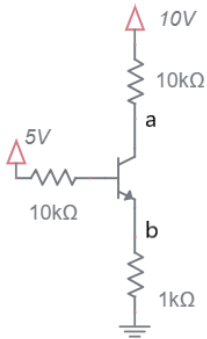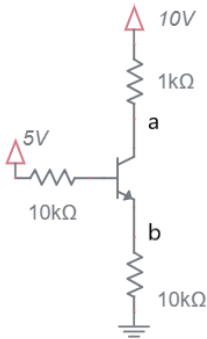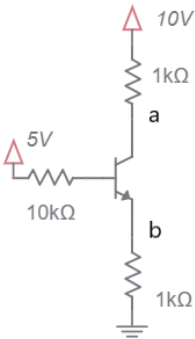


| Problem |  | a    | b    | ic      | ib      | ie      | $\beta$ |
|---------|--|------|------|---------|---------|---------|---------|
| 001     |  | 9.6V |      | 0.43mA  | 4.3uA   | 0.43mA  |         |
| 002     |  | 5.7V |      | 4.3mA   | 43uA    | 4.3mA   |         |
| 003     |  | 0.2V |      | 9.8mA   | 0.43mA  | 10.23mA | 23      |
| 004     |  | 9.4V |      | 0.6mA   | 6uA     | 0.6mA   |         |
| 005     |  | 4V   |      | 6mA     | 60uA    |         |         |
| 006     |  | 0.2V |      | 9.8mA   | 0.6mA   | 10.4mA  | 16      |
| 007     |  | 5.7V | 4.3V | 4.3mA   | 43uA    | 4.3mA   |         |
| 008     |  | 4.5V | 4.3V | 0.55mA  | 3.8mA   | 4.3mA   | 0.73    |
| 009     |  | 5.7V | 4.3V | 0.43mA  | 4.3uA   | 0.43mA  |         |
| 010     |  | 6.1V | 3.9V | 3.9mA   | 39uA    | 3.9mA   |         |
| 011     |  | 9.6V | 4.3V | 0.43mA  | 4.3uA   | 0.43mA  |         |
| 012     |  | 1.3V | 1.1V | 0.87mA  | 0.32mA  | 1.1mA   | 2.7     |
| 013     |  | 9.3V |      |         | unknown |         |         |
| 014     |  |      |      | unknown |         |         |         |
| 015     |  |      |      | 0.43mA  | 4.3uA   | 0.43mA  |         |
| 016     |  | 3.9V |      | 3.9mA   | 39uA    | 3.9mA   |         |
| 017     |  | 4.3V |      | 0.43mA  | 4.3uA   | 0.43mA  |         |

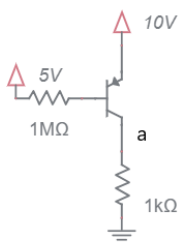
## DC circuits with PNP BJTs and resistors

Determine the voltage at the labeled nodes. Determine collector, base and emitter currents.


- If the BJT is in the active region, assume  $V_{eb} = 0.7V$ ,  $\beta = 100$ , and  $i_c = i_e$ .
- If the BJT is in saturation, assume that  $V_{ec} = 0.2V$ .
- Only compute  $\beta$  when the BJT is in saturation.
- Write your answers on the table shown on the page following the problems.
- On separate page(s), show your work for each problem. Denote the operating region of BJTs by writing ACT/SAT next to active/saturated mode BJTs respectively.
- Write "unknown" for circuits whose current/voltage cannot be determined.
- Round your answer to 2-significant figures and include units.




001

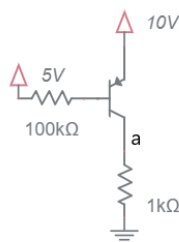


002

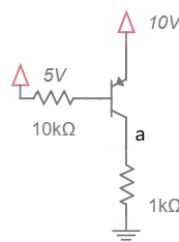


003

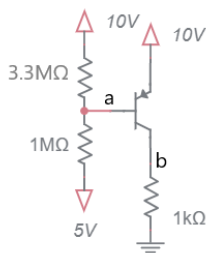


004

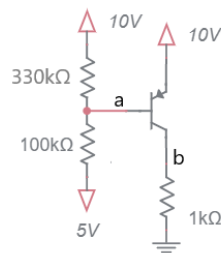


005

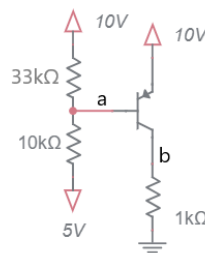


006

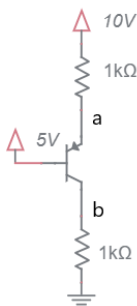


007

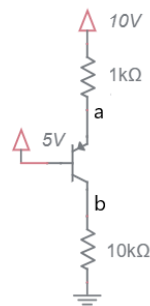


008

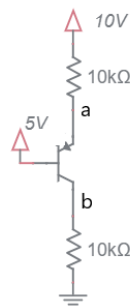


009

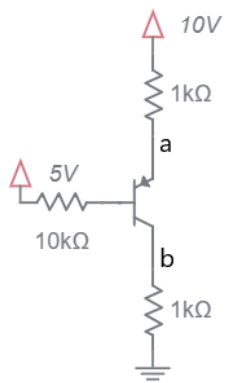


010

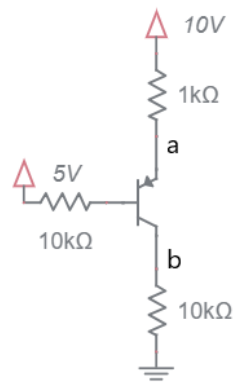


011

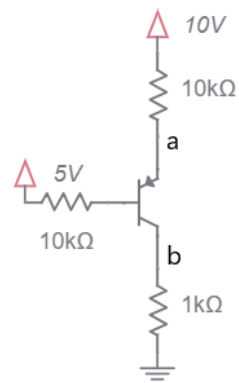


012

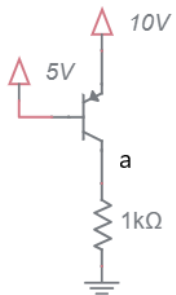

013

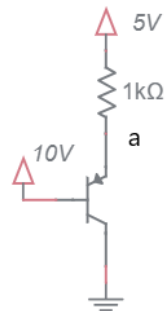

014

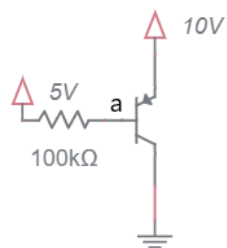

015

| Problem |  | a     | b     | ic      | ib     | ie      | $\beta$ |
|---------|--|-------|-------|---------|--------|---------|---------|
| 001     |  | 0.43V |       | 0.43mA  | 4.3uA  | 0.43mA  |         |
| 002     |  | 4.3V  |       | 4.3mA   | 43uA   | 4.3mA   |         |
| 003     |  | 9.8V  |       | 9.8mA   | 0.43mA | 10.2mA  | 23      |
| 004     |  | 9.3V  | 0.41V | 0.41mA  | 4.1uA  | 0.41mA  |         |
| 005     |  | 9.3V  | 4.1V  | 4.1mA   | 41uA   | 4.1mA   |         |
| 006     |  | 9.3V  | 9.8V  | 9.8mA   | 0.41mA | 10.2mA  | 24      |
| 007     |  | 5.7V  | 4.3V  | 4.3mA   | 43uA   | 4.3mA   |         |
| 008     |  | 5.7V  | 5.5V  | 0.55mA  | 3.8mA  | 4.3mA   | 0.15    |
| 009     |  | 5.7V  | 5.3V  | 0.53mA  | 5.3uA  | 0.53mA  |         |
| 010     |  | 6.1V  | 3.9V  | 3.9mA   | 39uA   | 3.9mA   |         |
| 011     |  | 6.3V  | 6.1V  | 0.61mA  | 3.1mA  | 3.7mA   | 0.2     |
| 012     |  | 5.7V  | 0.43V | 0.43mA  | 4.3uA  | 0.43mA  |         |
| 013     |  |       |       | unknown |        |         |         |
| 014     |  | 9.3V  |       |         |        | unknown |         |
| 015     |  | 9.3V  |       | 4.3mA   | 43uA   |         |         |