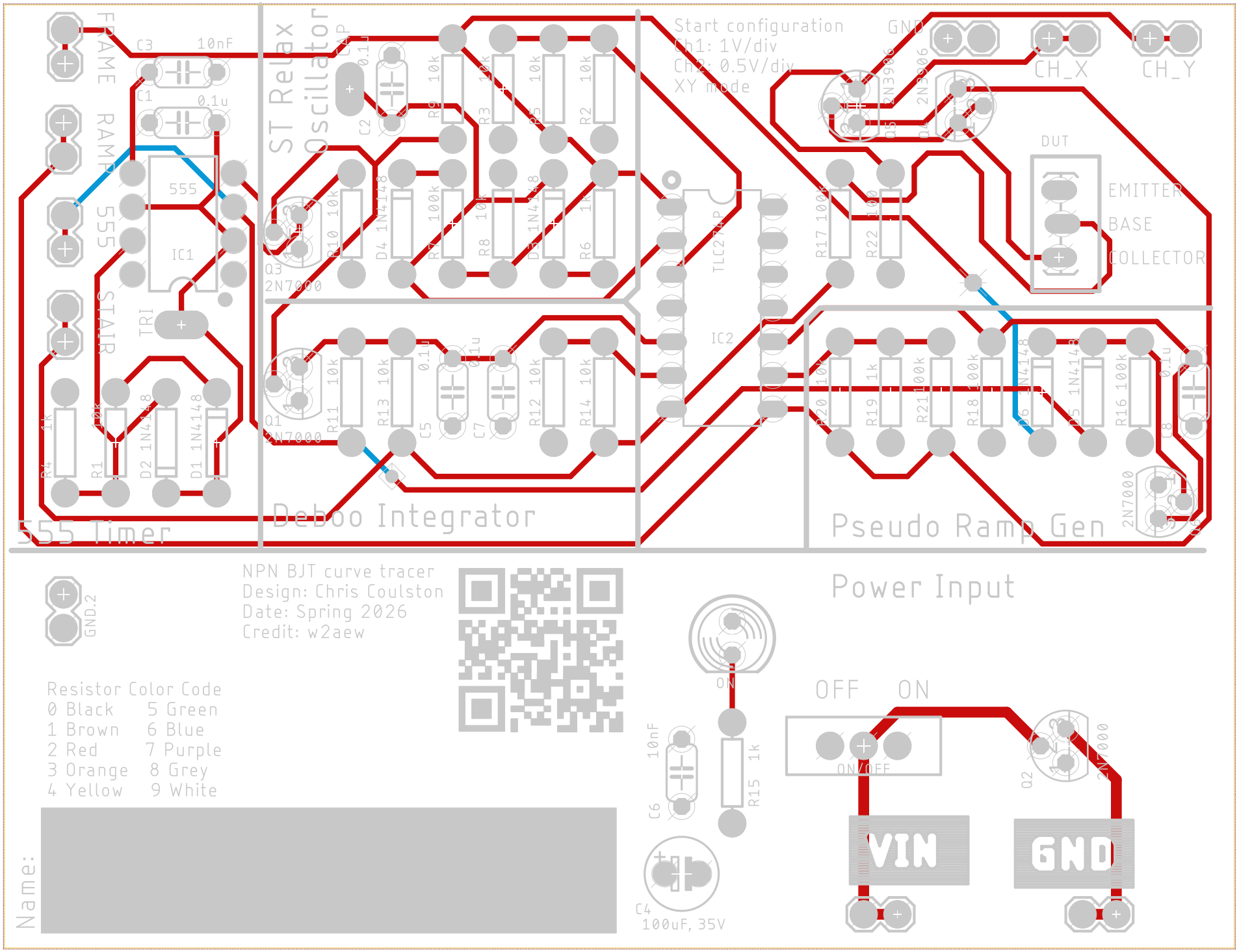

555 Timer
Deboo Integrator
Pseudo Ramp Gen
Power Input
NPN BJT curve tracer
Design: Chris Coulston
Date: Spring 2026
Credit: w2aew
Start configuration
Ch1: 1V/div
Ch2: 0.5V/div
XY mode
CH_X
CH_Y
GND
DUT
EMITTER
BASE
COLLECTOR
OFF ON
VIN
GND
Resistor Color Code
0 Black 5 Green
1 Brown 6 Blue
2 Red 7 Purple
3 Orange 8 Grey
4 Yellow 9 White
Name: